

## **DIGITAL SYSTEM**

### **2<sup>rd</sup> PRACTICUM: LOGIC GATES COMBINATION**




Writed by :

Name : Ainayah Syifa Hendri  
NIM : L200183203  
Major : Information Engineering

**INFORMATION TECHNOLOGY**  
**FACULTY OF COMMUNICATION AND INFORMATICS**  
**MUHAMMADIYAH UNIVERSITY OF SURAKARTA**  
**2019**

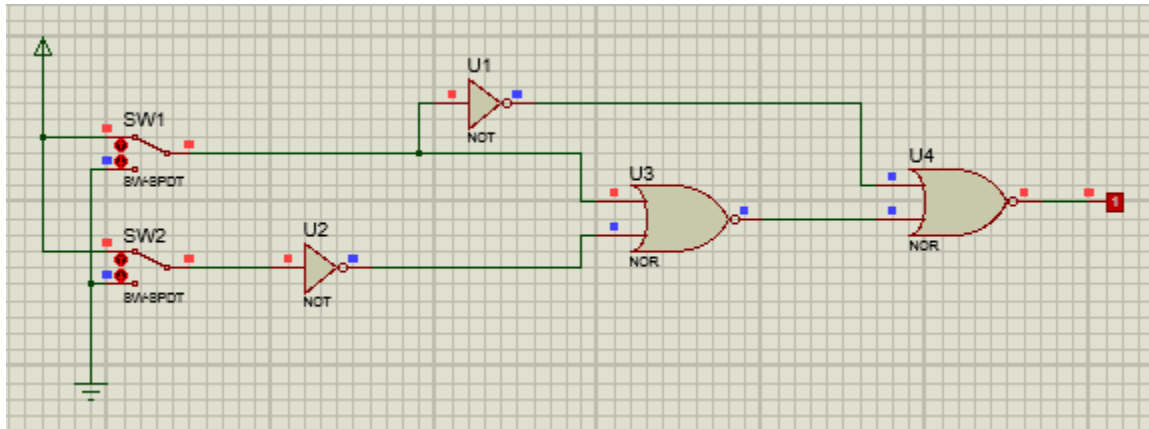1. Create a logic gate combination as shown in figure below !




a) Complete the truth table and time diagram based on the circuit above !

- Truth table

X	Y	L <sub>1</sub>
0	0	0
1	0	1
0	1	0
1	1	1

- Time diagram

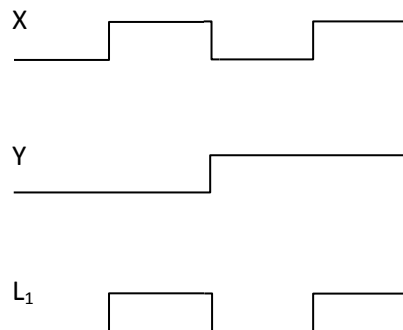

b) Boolean function :  $L_1 = X + \overline{Y} + \overline{X}$

2. Create the logic gate circuit based on the following Boolean function !

$$F = (\overline{\overline{A} \cdot B} + C) + (\overline{D} \cdot E)$$

