

DIGITAL SYSTEM

PRACTICUM REPORT 11 : REGISTER



NAME : AINAYAH SYIFA HENDRI

NIM : L200183203

INFORMATION TECHNOLOGY

FACULTY OF COMMUNICATION AND INFORMATICS

MUHAMMADIYAH UNIVERSITY OF SURAKARTA

2019

NIM : L200183203


NAME : AINAYAH SYIFA HENDRI

CLASS : X

ASSISTANT : SALSA SASMITA MUKTI

DATE OF PRACTICUM : Friday, June 21th 2019


#Exercise 1. 4-bit Register circuit

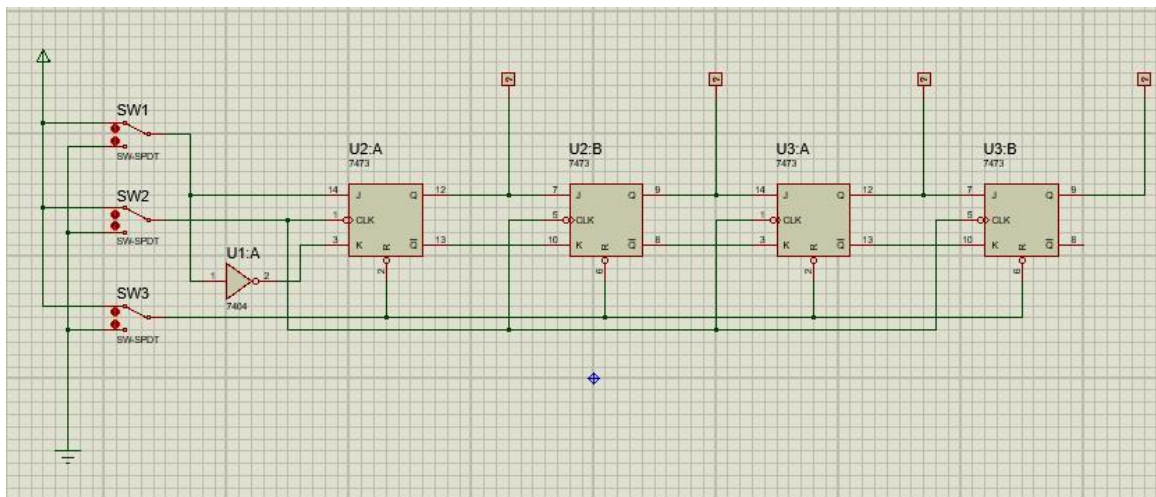

1. Reset the shift register by activating the SW3 switch (open).
2. Set SW1 switch in binary position 1.
3. Give 4 shear pulses (0-1) through the SW2 switch, observe the register state through the PROBE condition.
4. Record the binary number of the contents of the register after 4 slide pulses have been given.
ABCD = **1111**
5. Next, the SW1 switch sets at binary position 0, and gives 4 pieces of sliding pulses through the SW2 switch. And record the contents of the register. ABCD = **0000**

6. Using SW1 switch and SW2 switch.
Give the load on the shift register step by step through the procedure below:
SW1 = 1, then give one pulse from the SW2 switch (**1000**)
SW1 = 0, then give one pulse from the SW2 switch (**0100**)
SW1 = 1, then give one pulse from the SW2 switch (**1010**)
SW1 = 0, then give one pulse from the SW2 switch (**0101**)
7. After that, observe the PROBE state and write a decimal number that is equivalent to the binary number in the shift register.
Binary Numbers = **0101** Decimal Number = **5**

#Exercise 2. IC 74194 Register circuit

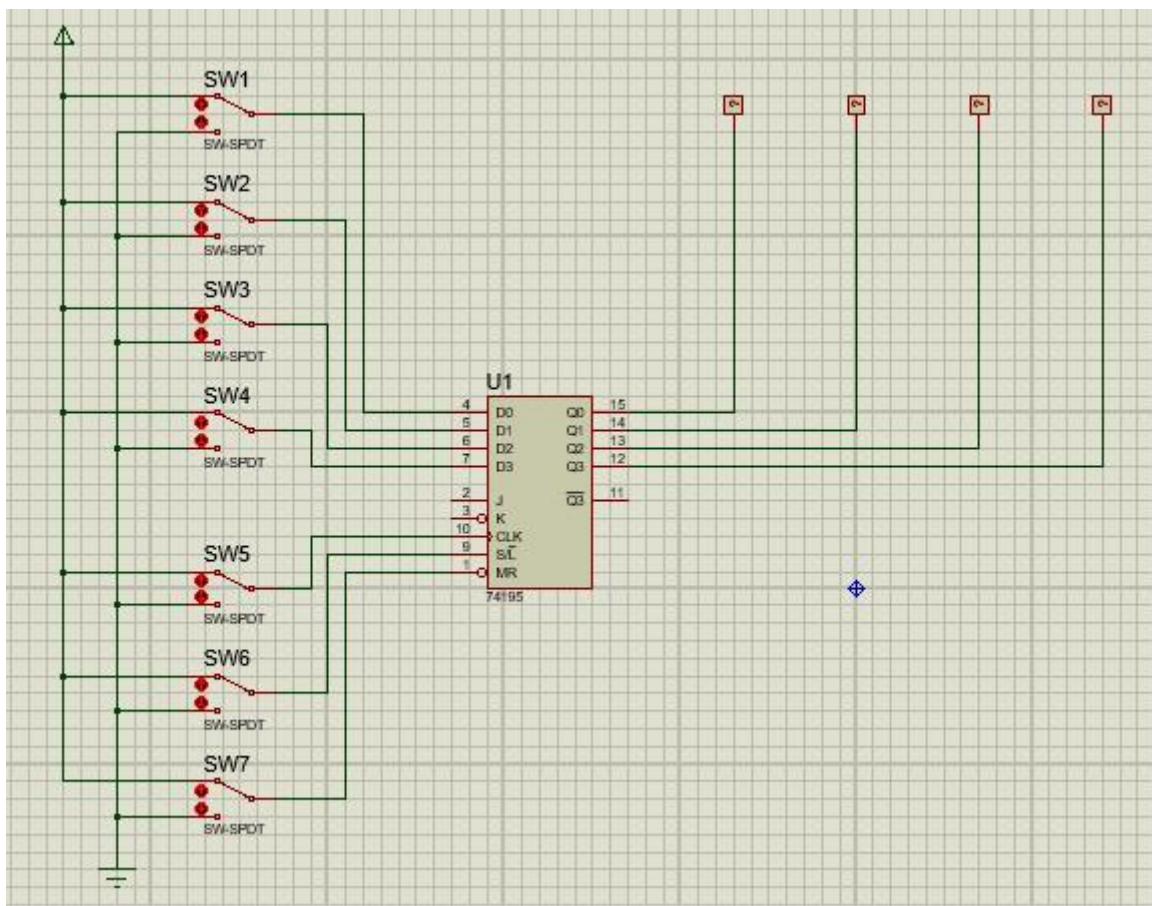

1. SW1, SW2, SW3 and SW4 data switches are used as parallel data sources. The SW5 switch is used to generate a sliding pulse.
The SW6 switch functions as the control mode for the circuit. The SW7 switch functions as a data reset.

2. Set all data switches (SW1 to SW4) to binary 0.
3. Set SW6 switch to binary 0, then the SW5 switch is set to 0 then set to 1 again (give a clock pulse), then return the SW6 switch to binary 1 again. note the state of PROBE X1, X2, X3, and X4.

ABCD = **0000**

4. Next, set all data switches (SW1 to SW4) to binary 1.
5. Set SW6 switch to binary 0, then the SW5 switch is set to 0 then set to 1 again (give a clock pulse), then return the SW6 switch to binary 1 again. note the state of PROBE X1, X2, X3, and X4.

ABCD : **1111**

6. Give a clock pulse (set 0 then set 1 again) on the SW5 switch 4 times and observe the PROBE state after you enter 4 pulses slide into the shift- register and record the results below.


After pulse 1: ABCD = **0111**

After pulse 2: ABCD = **1011**

After pulse 3: ABCD = **0101**

After pulse 4: ABCD = **1010**

#Exercise 3. Left Slide Register 1

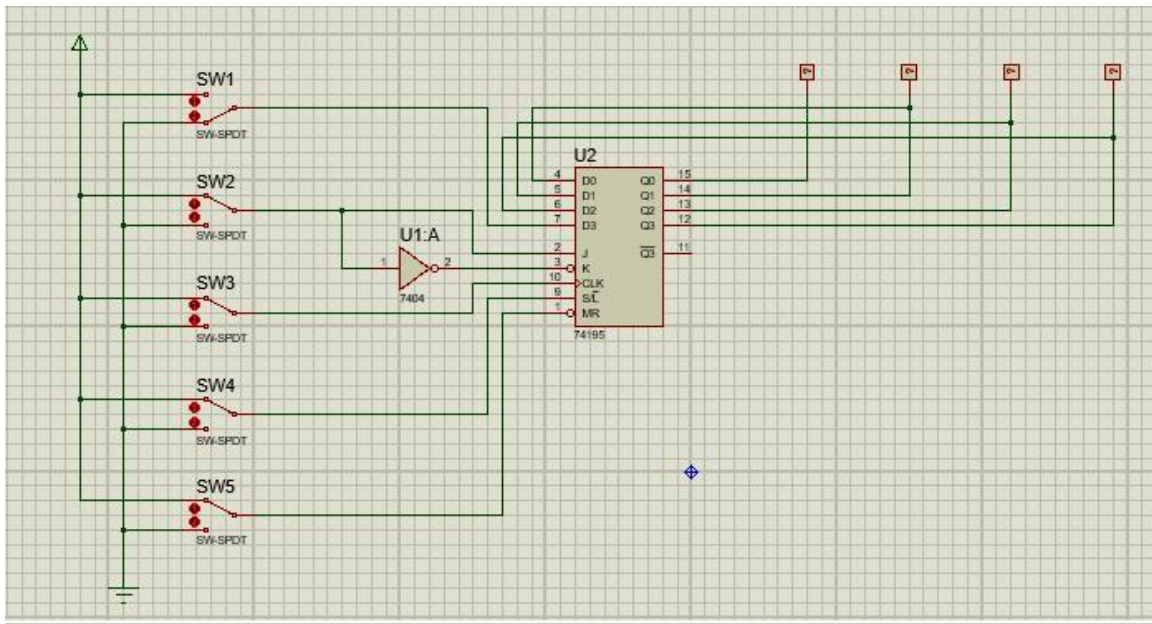

1. You can use the SW1 switch for serial data input in the left slide operation, the SW2 switch for serial data input in the right slide operation. The SW3 switch is used as the clock register source. The SW4 switch is used as the mode controller (control mode) of the circuit, which will determine the left or right sliding operation. SW5 switch to reset registers.
2. run the simulation.
3. Set the switch in the following binary conditions: SW1 = 0; SW2 = 0; SW3 = 1; SW4 = 0; SW5 = 1
4. To reset data, give input one pulse on SW5 (0 - 1).
5. Set SW1 to binary value 1.
6. Give pulses to the SW3 switch 5 times then record the results at the output. before the pulse is given: **ABCD = 0000**
after pulse 1: **ABCD = 0001**
after pulse 2: **ABCD = 0011**
after pulse 3: **ABCD = 0111**
after pulse 4: **ABCD = 1111**
after pulse 5: **ABCD = 1111**

7. Set the switch in the following binary conditions: SW1 = 0; SW2 = 0; SW3 = 1; SW4 = 1; SW5 = 1
8. To reset the data, give a pulse on the SW5 switch (set 0 then set 1 again).
9. Set the SW2 switch to binary 1.
10. Give pulses to the SW3 switch 5 times then record the results at the output. Before
Pulse Is Provided: **ABCD = 0000**
After pulse 1: **ABCD = 1000**
After pulse 2: **ABCD = 0100**
After pulse 3: **ABCD = 1010**
After pulse 4: **ABCD = 0101**
After pulse 5: **ABCD = 1010**
11. Set the switch in the following binary conditions:
SW1 = 0; SW2 = 0; SW3 = 1; SW4 = 0; SW5 = 1
12. To reset the data, give a pulse on the SW5 switch (set 0 then set 1 again).
13. Set the SW1 switch to binary 1.
14. Give pulses to the SW3 switch 1 time then record the results at the output. Before
Pulse Is Provided: **ABCD = 0000**
After Pulse Is Provided: **ABCD = 0001**
15. Set the SW1 switch to binary 0.
16. Give pulses to the SW3 switch 3 times then record the results at the output. After
pulse 1: **ABCD = 0010**
After pulse 2: **ABCD = 0100**
After pulse 3: **ABCD = 1000**
17. Set the SW4 switch to binary 0.
18. Give pulses to the SW3 switch 3 times then record the results at the output. After
pulse 1: **ABCD = 0000**
After pulse 2: **ABCD = 0000**
After pulse 3: **ABCD = 0000**

19. To better understand experiment 3, try to do other shift operations by changing the conditions of the SW1, SW2, SW3, SW4, and SW5 switches so that you understand the functions of each button.

Exercise 4. Left Slide Register 2

1. Set the switch in the following binary conditions:
SW1 = 0; SW2 = 0; SW3 = 1; SW4 = 0; SW5 = 1
To reset the data, give a pulse on the SW5 switch (set 0 then set 1 again).
2. Set the SW1 switch to binary 1.
3. Give pulses to the SW3 switch 2 times then record the results at the output.
 - Before Pulse Is Provided : ABCD = 0000 : Decimal number = **0**
 - After pulse 1 : ABCD = 0001 : Decimal number = **1**
 - After pulse 2 : ABCD = 0011 : Decimal number = **3**
4. Set the SW1 switch to binary 0.
5. Give pulses to the SW3 switch 1 times then record the results at the output. Before
6. Study the data you got in the procedure above! What is the relationship between the numbers obtained, when the register is loaded with data and the left shift operation register?
Answer : The number is obtained when SW5 is given input 1, the left sliding operation register applies if SW4 is given input 0, if SW1 is given input 1 when SW3 is given 1 pulse (from input 0 is changed to 1) it will produce output 1 on the right logicprobe. Likewise if SW1 is given input 0 then the output is 0. If SW3 is given 1 pulse again, the output will shift to the left. (increase)
7. What mathematical operation is formed by sliding left? Answer: **multiplication with value “and” x 2**
8. Set the switch in the following binary conditions: SW1 = 0; SW2 = 0; SW3 = 1; SW4 = 0; SW5 = 1.
9. To reset the data, give a pulse on the SW5 switch (set 0 then set 1 again).

10. Set the SW2 switch to binary 1.
11. Give pulses to the SW3 switch 1 times then record the results at the output. Before
Pulse Is Provided: **ABCD = 0000 : Decimal number = 0.**
After Pulse Is Provided: **ABCD = 1000 : Decimal number = 8.**
12. Set the SW2 switch to binary 0.
13. Give pulses to the SW3 switch 1 times then record the results at the output. After
14. Set the SW2 switch to binary 1.
15. Give pulses to the SW3 switch 1 times then record the results at the output. After
16. Give pulses to the SW3 switch 1 times then record the results at the output.
After Pulse Is Provided : **ABCD = 1101 Decimal number = 13**
17. Learn the data that you have obtained, What is the relationship between the numbers obtained, when the register is loaded with data and the left shift operation register?
Answer : The number is obtained when SW5 is given input 1, the right sliding operation register applies if SW4 is given input 1, if SW2 is given input 1 when SW3 is given 1 pulse (from input 0 is changed to 1) it will produce output 1 on the left logicprobe. Likewise if SW2 is given input 0 then the output is 0. If SW3 is given 1 pulse again, the output will shift to the right. (decrease)
18. What mathematical function is formed, when right sliding operation occurs?
Answer : division with value "***and***" / 2.