

DIGITAL SYSTEM

6th PRACTICUM: KARNAUGH MAP



Written by :

Name : Ainayah Syifa Hendri
NIM : L200183203
Major : Information Engineering

INFORMATION TECHNOLOGY
FACULTY OF COMMUNICATION AND INFORMATICS
MUHAMMADIYAH UNIVERSITY OF SURAKARTA
2019

PRACTICUM ACTIVITIES

1st Experiment

1. Create a combination of logic gates based on the following karnaugh map.

		AB			
		00	01	11	10
CD	00	0	0	0	0
	01	1	1	1	0
	11	0	1	1	1
	10	0	0	0	0

I = 0101 II = 0001 III = 1111

1101 0101 1011


0111 A'C'D ACD

1111

BD

2. Boolean function: $F = BD + A'C'D + ACD$

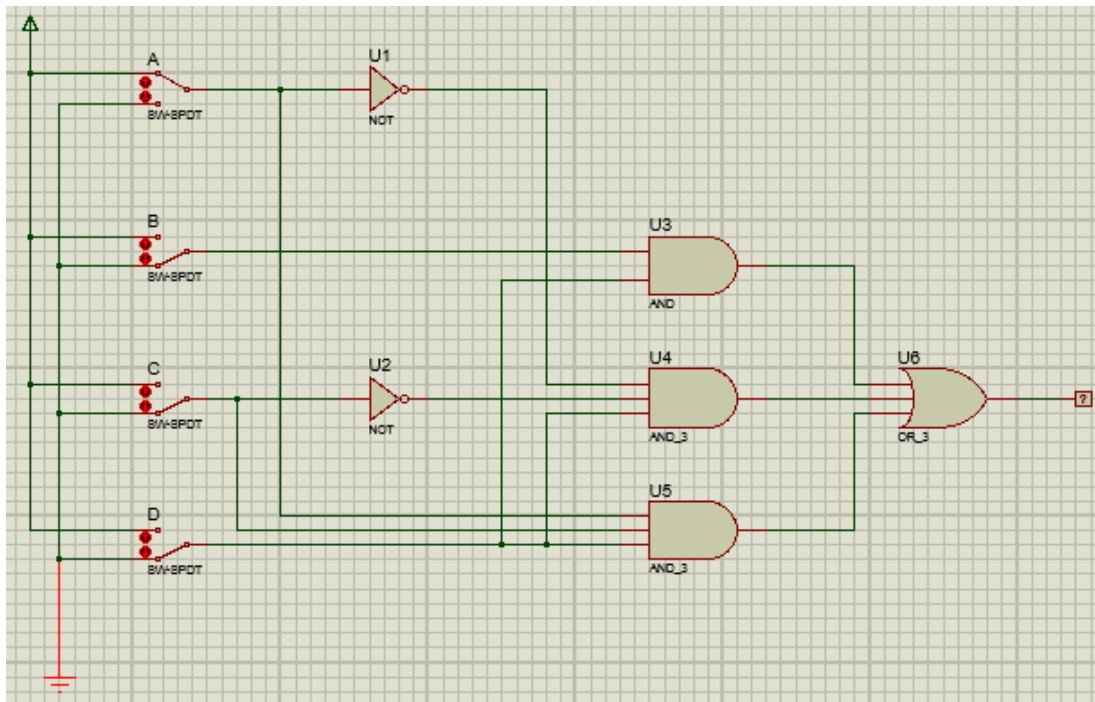3. Create logic gates based on your boolean function! Picture in the box below!



2nd Experiment

1. Create a combination of logic gates based on the following karnaugh map.

		AB			
		00	01	11	10
CD	00	1	0	0	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	0	0	1

- SOP : I = 0101 II = 0000

1101 1000

0111 0010

1111 1010

BD **B'D'**

- POS : I = 0100 II = 0001

1100 0011

0110 1001

1110 1011


B' + D **B + D'**

2. Boolean function: **F = BD + B'D'** (AND – OR)


$$\mathbf{F = (B' + D)(B + D') \text{ (OR – AND)}}$$

3. Create logic gates based on your boolean function! Picture in the box below!

- SOP

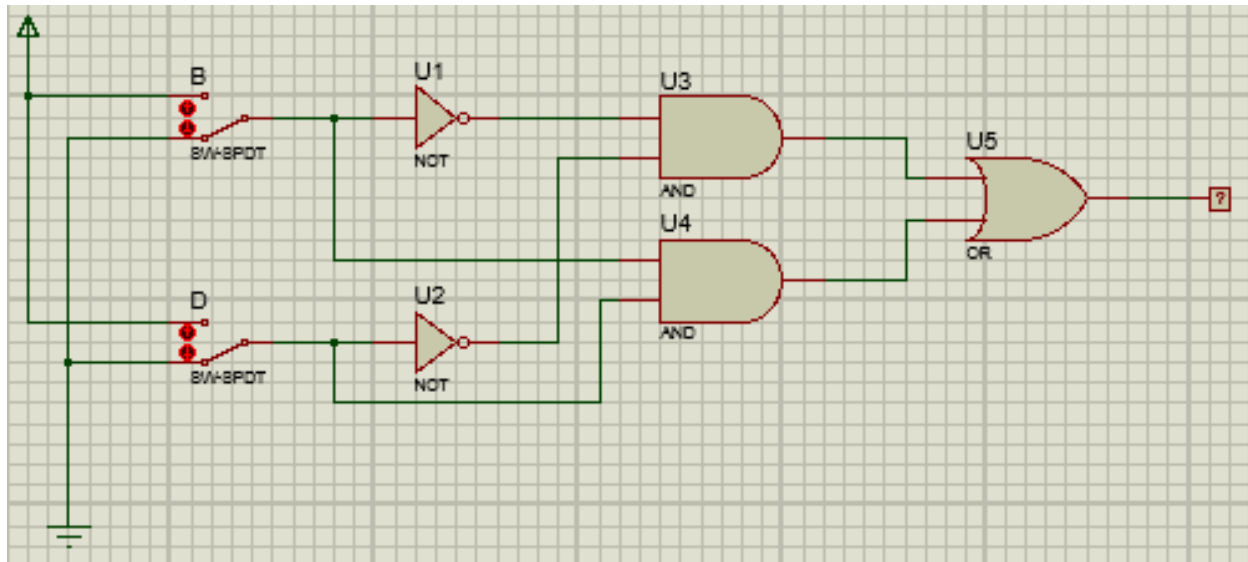

- POS

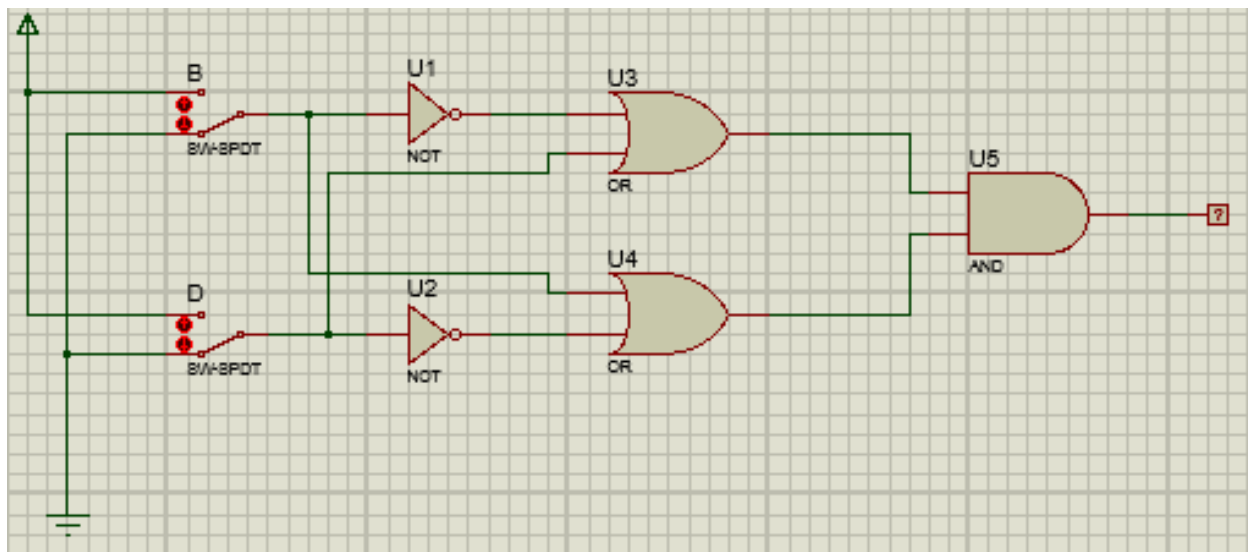

Do the two combinations give the same results? Yes / No

- SOP : $F = BD + B'D'$

- POS : $F = (B' + D)(B + D')$

$$= B'B + B'D' + BD + DD'$$

$$= 0 + B'D' + BD + 0$$

$$= BD + B'D'$$

So, the two combinations give the same results

3rd Experiment

1. Boolean function: $F = XYZ + XYZ' + XY'Z + X'YZ + X'YZ' + XY'Z' + X'Y'Z'$
2. Based on the boolean function, fill in the points on the map because of the following!

		XY			
		00	01	11	10
Z	0	1	1	1	1
	1	0	1	1	1

$$I = 010 \quad II = 110 \quad III = 000$$


$$110 \quad 100 \quad 010$$

$$011 \quad 111 \quad 110$$

$$\frac{111}{Y} \quad \frac{101}{X} \quad \frac{100}{Z'}$$

3. Simplify boolean functions : $F = X + Y + Z'$

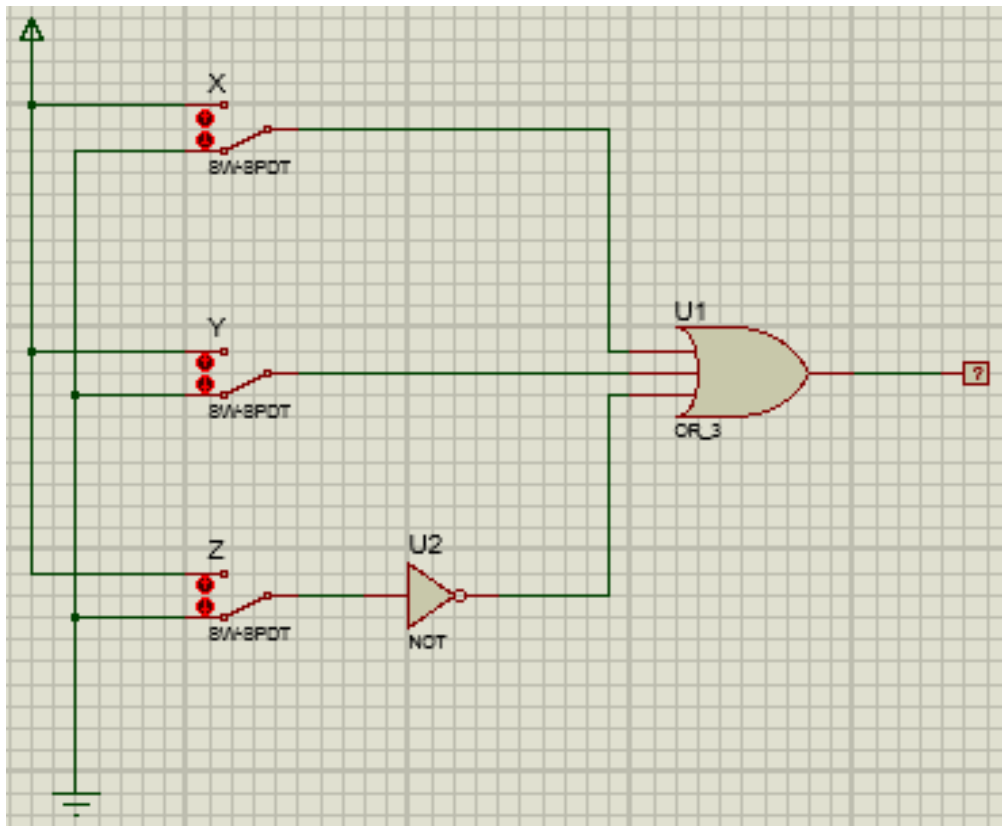4. Create logic gates based on your boolean function! Picture in the box below!




4th Experiment

1. Boolean function: $F = AD' + ABC + ABC' + BCD + BC'D' + AB'CD'$.
2. Based on the boolean function, fill in the points on the map because of the following!

		AB			
		00	01	11	10
CD	00	0	1	1	1
	01	0	0	1	0
	11	0	1	1	0
	10	0	0	1	1

I = 0100	II = 0111	III = 1100	III = 1100
<u>1100</u>	<u>1111</u>	1000	1101
BC'D'	BCD	1110	1111
		<u>1010</u>	<u>1110</u>
		AD'	AB

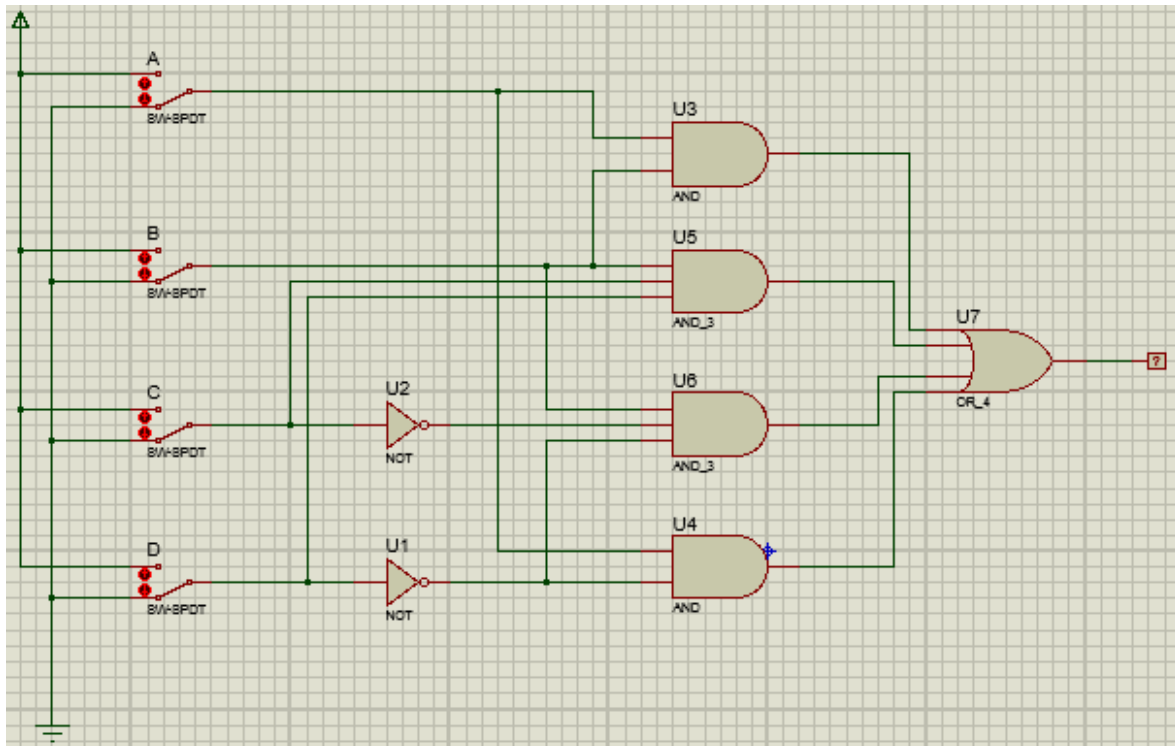3. Simplify boolean functions : $F = BC'D' + BCD + AD' + AB$
4. Create logic gates based on your boolean function! Picture in the box below!



5th Experiment

1. Boolean Function Table :

A	B	C	D	F
0	0	0	0	1
1	0	0	0	0
0	1	0	0	0
1	1	0	0	1
0	0	1	0	1
1	0	1	0	1
0	1	1	0	0
1	1	1	0	0
0	0	0	1	1
1	0	0	1	1
0	1	0	1	0
1	1	0	1	1
0	0	1	1	1
1	0	1	1	0
0	1	1	1	1
1	1	1	1	0


2. Based on the boolean function, fill in the points on the map because of the following!

		AB			
		00	01	11	10
CD	00	1	0	1	0
	01	1	0	1	1
	11	1	1	0	0
	10	1	0	0	1

I = 0000	II = 0011	III = 0010	IV = 1101	V = 1100
0001	0111	1010	1001	1101
0011	<u>A'CD</u>	<u>B'CD'</u>	<u>AC'D</u>	<u>ABC'</u>
0010				
<u>A'B'</u>				

3. Simple boolean function : $F = A'B' + A'CD + B'CD' + AC'D + ABC'$

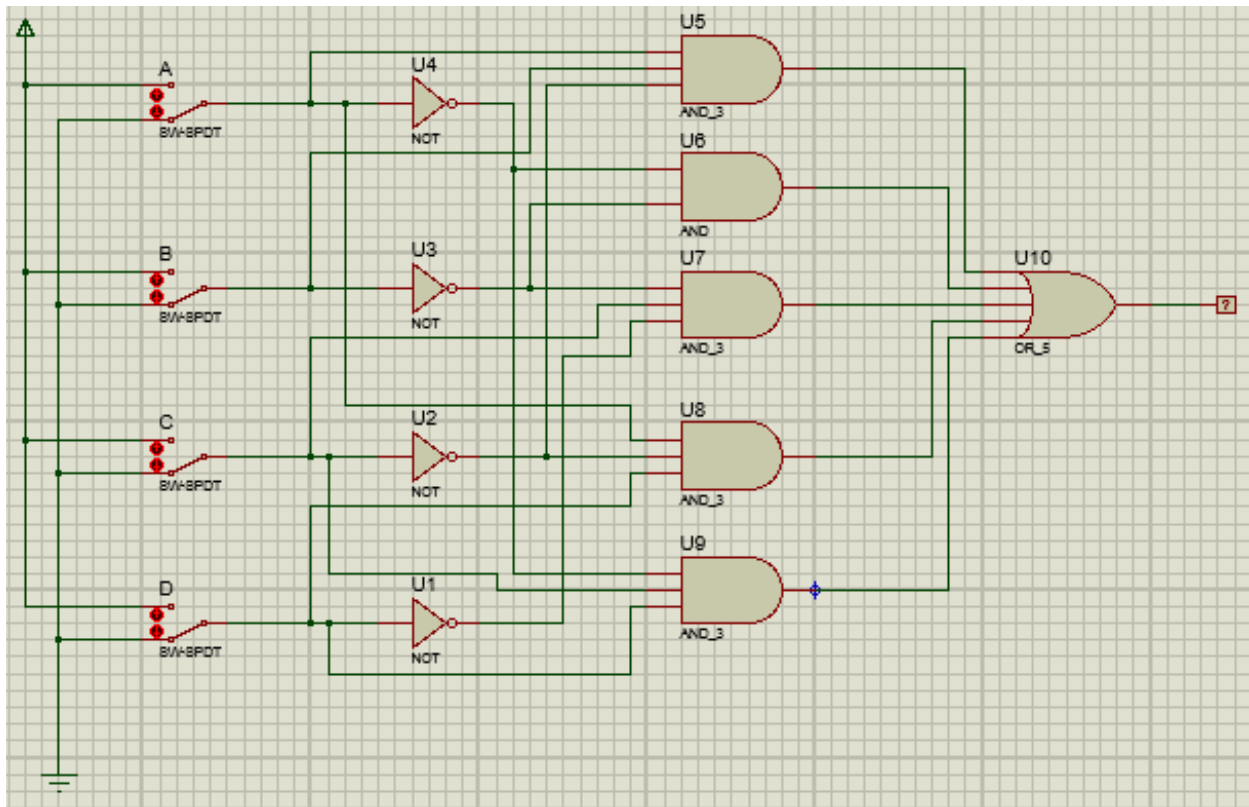4. Create logic gates based on your boolean function! Picture in the box below!



Do the two combinations give the same results? Yes / No